

Solenoids

Sauter/AD508/S08/based on T. Igoe: Physical Computing + <http://arduino.cc>

tutorials

Circuit:


http://www.arduino.cc/playground/uploads/Learning/solenoid_driver.pdf

General intro analog+digital input+output:


http://www.tinker.it/en/uploads/v3_arduino_small.pdf

Solenoids

- push-type

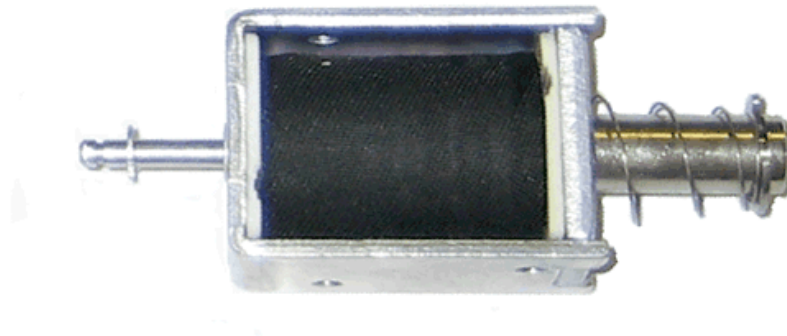

- pull-type

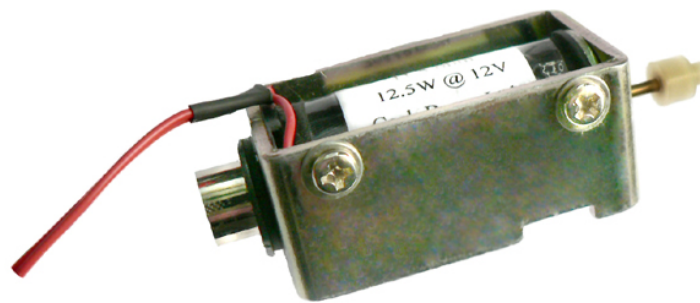

Note:

Both types require a mechanism (spring etc.) to move the shaft back into the rest position.

Reversing the polarity will not turn a push-type into a pull-type solenoid

Duty cycle + Maximum on time

duty cycle:

sum of on time plus off time

for instance: the solenoid is on for 1 second, and off for 2 seconds, the duty cycle is $1 / 1 + 2 = 1 / 3 = 0.33 = 33 \%$

maximum on time:

after which the solenoid must be turned off for the rest of the duty cycle

If a solenoid has a 20 % duty cycle

and the maximum on time of 0.1 seconds

then it cannot be turned on for more than 0.1 seconds every half second

$$20\% = 1 / 5 = 1 / 1_part_on + 4_parts_off$$

$$1_part_on = 0.1 \text{ sec}$$

$$4_parts_off = 4 \times 0.1 = 0.4 \text{ sec}$$

duty cycle: 0.5 sec

Arduino Code


(Solenoid controlled by push button, see circuit diagram next page)

```
int ledPin = 13;           // onboard LED
int inputPin = 2;          // input pin
int outPin = 0;
int state = 0;             // pin status

void setup() {
  pinMode(ledPin, OUTPUT);  // declare LED as output
  pinMode(outPin, OUTPUT);  // declare outPin as output
  pinMode(inputPin, INPUT); // declare pushbutton as input
}

void loop(){
  state = digitalRead(inputPin); // read input value
  if (state == HIGH) {           // check if the input is HIGH
    digitalWrite(ledPin, LOW);   // turn LED OFF
    digitalWrite(outPin, LOW);   // turn Solenoid OFF
  } else {
    digitalWrite(ledPin, HIGH);  // turn LED ON
    digitalWrite(outPin, HIGH);  // turn Solenoid OFF
  }
}
```

How to Drive Solenoids with the Arduino

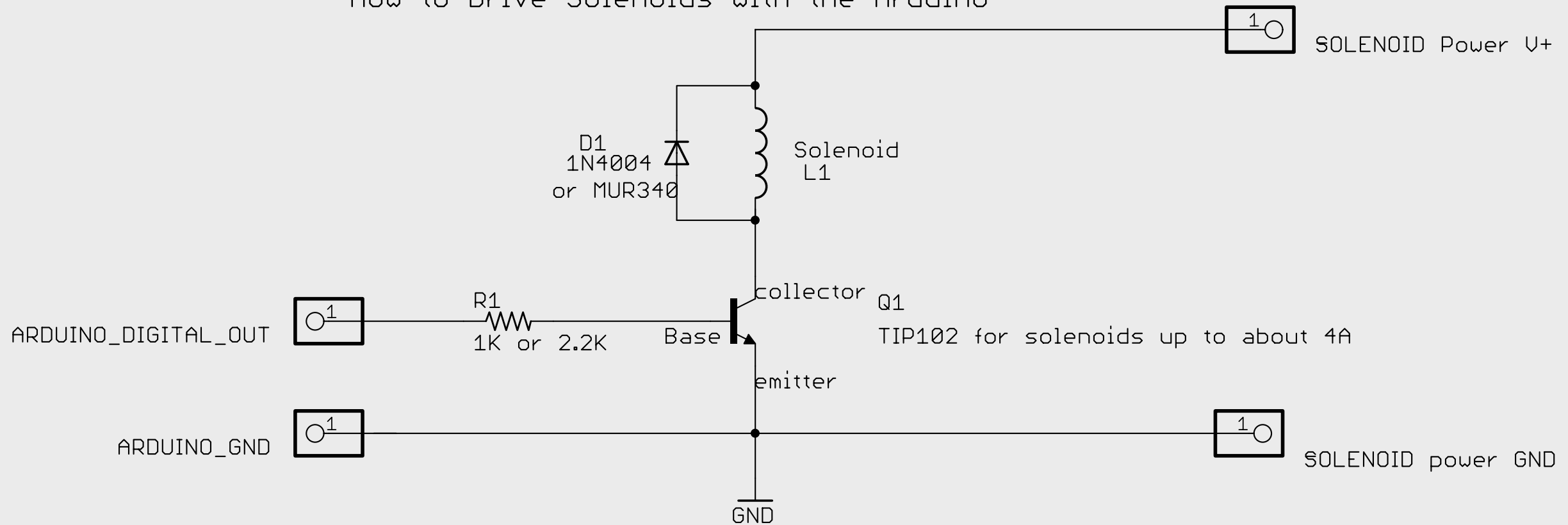

Notes:

- you will most likely need a heat sink on the transistor.
- This diagram is for DC solenoids rated up to about 24W: i.e. 12V@2A, 6V@4A, 24V@1A etc.
- The protection diode should preferably be a schottky type, which has better response times. Something like a MUR340 is good for loads up to 3A.